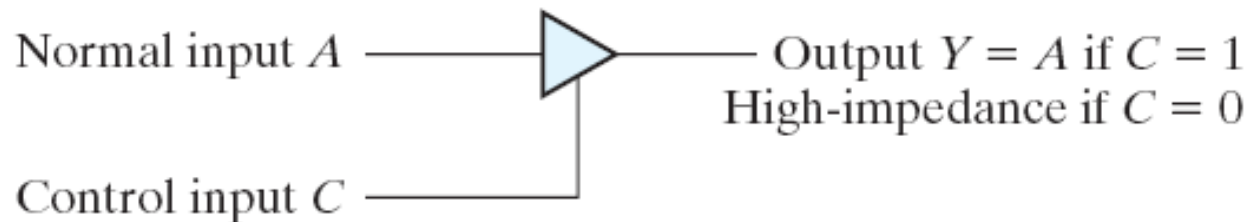


# Digital VLSI Circuits and HDL





Mazad S. Zaveri, PhD

# Tri-state buffer

- Has three output states (depending on the control signal)
  - Logic 1
  - Logic 0
  - Floating node (high-impedance to both GND and VDD)
    - Also means the output **node** is not driven to either logic 0 state or logic 1 state
- One can assume that the buffer shown below, is a switch, that connects or disconnects the **node A** to **node Y** depending on the value of the switch **control C**



# Controlled buffer/inverter

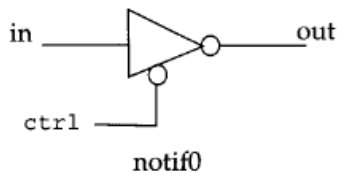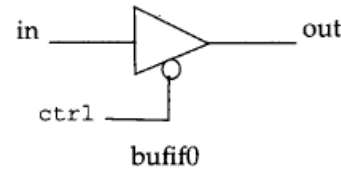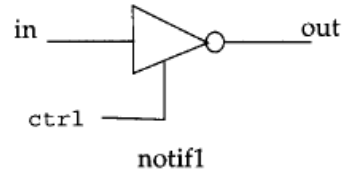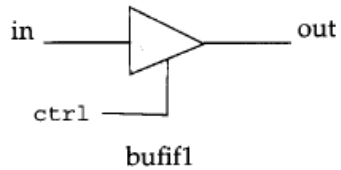

		ctrl			
bufif1		0	1	x	z
in	0	z	0	L	L
	1	z	1	H	H
	x	z	x	x	x
	z	z	x	x	x

		ctrl			
bufif0		0	1	x	z
in	0	0	z	L	L
	1	1	z	H	H
	x	x	z	x	x
	z	x	z	x	x

		ctrl			
notif1		0	1	x	z
in	0	z	1	H	H
	1	z	0	L	L
	x	z	x	x	x
	z	z	x	x	x

		ctrl			
notif0		0	1	x	z
in	0	1	z	H	H
	1	0	z	L	L
	x	x	z	x	x
	z	x	z	x	x

```
//Instantiation of bufif gates
bufif1 b1 (out, in, ctrl);
bufif0 b0 (out, in, ctrl);
```

```
//Instantiation of notif gates
notif1 n1 (out, in, ctrl);
notif0 n0 (out, in, ctrl);
```

The L and H symbols have a special meaning. The L symbol means that the output has 0 or z value. The H symbol means that the output has 1 or z value. Any transition to H or L is treated as a transition to x.